

---

# Title: Noise Detector

---

- By Mohd Assad Shamim
- Admission No. : 23JE0598

## **PROJECT CONCEPT:**

This project mainly focuses on creating a low-cost, sound-activated switching circuit using a microphone, transistors, and a 555 timer IC. The primary goal is to detect clapping or any sudden noise and convert that acoustic signal into an electrical signal which, after amplification and conditioning, triggers a desired output. This output could be used to light up an LED, activate a buzzer, or even control home appliances like fans and lamps with a relay. The entire project is implemented on a breadboard and powered by a 9V battery, making it simple, portable, and ideal for beginners and educational demonstrations.

## **Working Principle:**

- **Microphone Detection**

A condenser microphone detects the clap sound and converts it into an electrical signal. This signal is very weak, so it needs to be amplified.

- **BC547 Transistor Amplification**

The weak signal from the microphone is fed into the base of a BC-547 transistor. The transistor amplifies this signal and produces a larger voltage pulse at its collector. Cascading amplifier is used to do even more amplification. This amplified signal acts as a trigger for the 555 timer IC.

- **555 Timer for generating delay**

The 555 timer is configured in monostable mode to respond to the amplified pulse. In monostable mode, the output stays ON for a fixed time and then turns OFF automatically depending upon the value of resistor and capacitor.

## Components required:

- 555 timer IC (1).
- N-P-N transistors BC-547 (2).
- Resistors: 3.3K $\Omega$ , 100K $\Omega$ , 270 $\Omega$ , 470 $\Omega$ , 1K $\Omega$ , 1.5K $\Omega$ .
- Capacitor: 22 $\mu$ F, 100nF (code- 104).
- LED (1).
- Microphone (1).
- Breadboard (1).
- Battery 9V (1).
- Connecting wires.

## Circuit Wiring:

- **Microphone Section:**
  - Connect one terminal of the microphone to the base of the first BC547 transistor through a resistor.
  - The other microphone terminal is grounded.
  - The collector of the transistor goes to Vcc through a resistor, and the emitter is grounded.
- **Amplification Section:**
  - The output from the collector of the first transistor is sent to the base of a second BC547 transistor for further amplification.
  - This cascaded setup improves the signal quality to trigger the timer accurately.
- **Timer and Output Section:**
  - The amplified signal is sent to the trigger pin (pin 2) of the 555 timer IC configured in **monostable mode**.
  - The output pin (pin 3) is connected to an LED (via a resistor) or to a relay for switching higher power devices.
  - Proper capacitor and resistor values at pin 6 & 7 define the ON-time duration.
- **Power Supply:**
  - All active components are powered through a standard 9V battery.
  - Power rails on the breadboard are used to distribute Vcc and GND efficiently.

## Outcomes and Applications:

- **Energy-Efficient Switch:**

Since the 555 timer remains OFF until a sound is detected, the circuit **saves power**.

- **Automation Possibilities:**

By **replacing the LED with a relay**, this circuit can control **appliances** like **lights, fans, or other electronic devices**.

## Practical Applications:

- Sound-activated light or fan control systems
- Home automation (clap-to-switch appliances)
- Noise detection for security alarms
- Interactive toys or sound-based triggers in art installations
- Assistive devices for differently-abled individuals

### **Circuit diagram:**

